

## **Operational amplifier**

Kevin Mika  
kevin.mika@tu-dortmund.de

Noah Krystiniak  
noah.krystiniak@tu-dortmund.de

Execution: 13.11.2018


# Contents

1	Execution
---	-----------

1
---


## 1 Execution

In order to determine the frequency response, a negative feedback operation amplifier as shown in Figure 1 is set up, which is adjusted via the negative feedback branch. The output voltage and the input voltage are graphically displayed on an oscilloscope. To

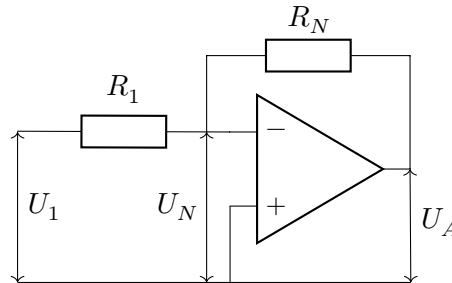


**Figure 1:** Feedback inverting linear amplifier.

determine the terminal voltage, use the circuit shown in Figure 1 and a non-inverting electrometer amplifier shown in Figure 2. The circuitry is then used to determine the terminal voltage. Circuit 3 is constructed to integrate input signals using the operational

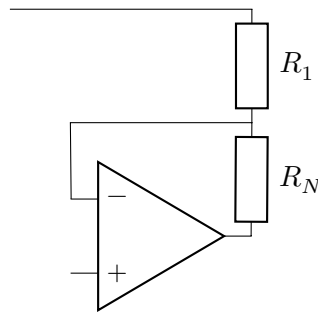


**Figure 2:** Non-inverting electrometer amplifier.

amplifier. In order to differentiate an input signal, the resistor and capacitor in Figure 3

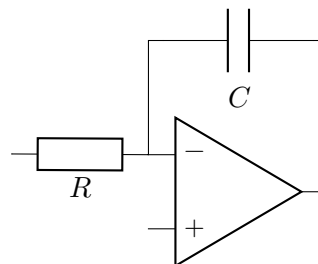


**Figure 3:** Reverse integrator.

are swapped according to Figure 4. The Schmitt trigger which works as a switch because

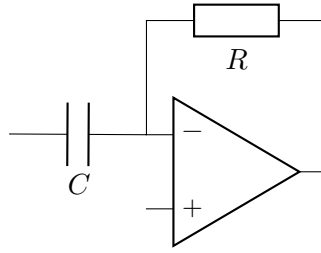**Figure 4:** Reverse integrator.

the output voltage changes its sign when the input voltage falls under the following condition:

$$\frac{-R_1}{R_p} U_B \quad (1)$$

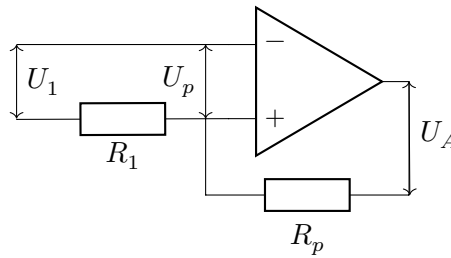**Figure 5:** Schmitt-trigger